# Project 60: Low-Power Divider A Comprehensive Study of Advanced Digital Circuits

By: Abhishek Sharma , Ayush Jain , Gati Goyal, Nikunj Agrawal

Documentation Specialist: Dhruv Patel & Nandini Maheshwari

Created By Teath Alpha

# Contents

1	Project Overview
2	Low-Power Divider2.1 Key Components of Low-Power Divider2.2 Working of Low-Power Divider2.3 RTL Code2.4 Testbench
3	Results 3.1 Simulation
4	Advantages of Low-Power Divider
5	Disadvantages of Low-Power Divider
6	Applications of Low-Power Divider
7	Conclusion
8	FAOs

Created By Teath Alpha

# 1 Project Overview

A low-power divider is a digital or analog circuit designed to perform division operations with minimal power consumption. In digital integrated circuits, especially for applications like mobile devices and IoT (Internet of Things) devices, power efficiency is crucial to prolong battery life and reduce heat. Dividers are often implemented in hardware for applications like DSP (Digital Signal Processing), control systems, and image processing, where frequent division operations are required.

### 2 Low-Power Divider

## 2.1 Key Components of Low-Power Divider

### Operand Registers:

- Hold the dividend and divisor values, readying them for the division process.
- Typically use low-power flip-flops or registers to reduce static and dynamic power consumption.

#### Control Unit:

- Manages the sequence of operations (e.g., partial quotient estimation, remainder updating).
- Coordinates low-power techniques like clock gating, ensuring only active components consume power.

### Partial Quotient Generator:

- Determines partial quotient bits iteratively or in parallel, based on the division algorithm.
- Optimized for minimal switching activity to save power during quotient generation.

### Remainder Calculation Logic:

- Computes and updates the remainder as the division progresses.
- May use techniques like non-restoring division or approximate calculation to reduce computational steps and save power.

### **Clock Gating and Operand Gating Circuits:**

- Clock gating selectively disables the clock signal to inactive parts of the divider.
- Operand gating ensures that only the necessary parts of the circuit are active based on the input operands.

### Pipeline Stages (if pipelined):

- Break down the division operation into stages, each handling a specific part of the calculation.
- Enable a balanced operation that saves power by keeping active stages at lower voltages when possible.

### **Power-Gating Transistors:**

- Shut down sections of the divider circuit not in use, reducing leakage power.
- Commonly used to turn off the divider entirely when idle.

### Voltage and Frequency Scaling Modules:

• Control circuits to dynamically adjust the divider's operating voltage and clock frequency.

• Used to reduce power during lower-performance needs or when accuracy is less critical.

### Approximation Logic (for approximate dividers):

- Used in approximate dividers where minor errors are acceptable.
- Simplifies the division process by reducing precision, leading to faster, lower-power operations.

### Output Registers:

- Store the final quotient and remainder results.
- Often use low-power registers, especially if the divider is part of a battery-operated or power-sensitive application.

### 2.2 Working of Low-Power Divider

### **Initialize Operands:**

- The divider circuit receives the dividend and divisor as inputs.
- Pre-processing may occur to prepare the operands, such as aligning bit widths if necessary.

### Choose Division Algorithm:

- Depending on the type, the divider uses an efficient algorithm (e.g., digit recurrence, non-restoring, or approximate methods).
- This choice impacts the power, speed, and accuracy of the operation.

### Partial Quotient Estimation (in iterative methods):

- The circuit estimates the next partial quotient bit(s) based on the current remainder and divisor.
- For digit recurrence methods, partial quotient values are generated incrementally, reducing unnecessary calculations.

### Reduce Remainder:

- The estimated partial quotient is used to update the remainder by subtracting or adding a scaled divisor.
- If using non-restoring division, remainders may be adjusted without performing a full restore operation, saving power.

### Apply Low-Power Techniques:

- Clock Gating: Parts of the divider not in use are disabled to reduce dynamic power.
- Operand Gating: Logic gates turn off when operand values don't change, preventing unnecessary switching.
- Voltage/Frequency Scaling: If speed is not critical, voltage and clock frequency are scaled down to reduce power consumption.

### Pipeline Stages (if pipelined):

- Intermediate stages hold results temporarily, enabling each stage to work on a different part of the division process.
- This helps balance power and performance but is only employed when power savings outweigh added pipeline costs.

### Check for Completion:

- The divider checks if the remainder is small enough to complete the division process.
- For iterative methods, this involves reaching a set number of iterations or achieving the desired precision.

### Post-Processing and Rounding:

- If needed, the result is rounded or normalized based on the application's precision requirements.
- For approximate dividers, additional steps might be taken to reduce error margins in the output.

### **Output Result:**

- The final quotient and remainder (if required) are output as the division result.
- In cases with power-gating, the divider is powered down after the result is produced.

### Power-Gating Unused Parts:

• Any parts of the circuit not needed post-calculation are completely powered off to reduce static (leakage) power consumption.

### 2.3 RTL Code

Listing 1: Low-Power Divider

```
3 module LowPowerDivider #(parameter WIDTH = 8) (
      input logic clk, reset,
      input logic [WIDTH-1:0] dividend, divisor,
      output logic [WIDTH-1:0] quotient, remainder,
      output logic valid
8 );
      always_ff @(posedge clk or posedge reset) begin
9
          if (reset) begin
               quotient <= 0; remainder <= 0; valid <= 0;
          end else if (divisor != 0) begin
12
               quotient <= dividend / divisor;</pre>
               remainder <= dividend % divisor;</pre>
14
               valid <= 1;</pre>
15
          end else begin
               quotient <= 0; remainder <= dividend; valid <= 0; //
17
                  Handle division by zero
          end
      end
20 endmodule
```

### 2.4 Testbench

Listing 2: Low-Power Divider

```
module LowPowerDivider_tb;

parameter WIDTH = 8;

logic clk = 0, reset;

logic [WIDTH-1:0] dividend, divisor, quotient, remainder;

logic valid;
```

```
LowPowerDivider #(.WIDTH(WIDTH)) uut (.clk(clk), .reset(reset),
         .dividend(dividend),.divisor(divisor), .quotient(quotient),
         .remainder(remainder), .valid(valid));
      always #5 clk = ~clk; // Clock generation
11
      initial begin
13
          reset = 1; #10 reset = 0;
          dividend = 16; divisor = 4; #10;
          $display("Div=%0d, Divisor=%0d, Quot=%0d, Rem=%0d, Valid=%b",
             dividend, divisor, quotient, remainder, valid);
          dividend = 15; divisor = 0; #10;
          $display("Div=%0d, Divisor=%0d, Quot=%0d, Rem=%0d, Valid=%b",
19
             dividend, divisor, quotient, remainder, valid);
          dividend = 12; divisor = 3; #10;
          $display("Div=%0d, Divisor=%0d, Quot=%0d, Rem=%0d, Valid=%b",
             dividend, divisor, quotient, remainder, valid);
          $finish;
      end
25 endmodule
```

# 3 Results

### 3.1 Simulation

 


Figure 1: Simulation of Low-Power Divider

# 3.2 Schematic

 


Figure 2: Schematic of Low-Power Divider

# 3.3 Synthesis Design

 


Figure 3: Synthesis Design of Low-Power Divider

# 4 Advantages of Low-Power Divider

### **Reduced Power Consumption:**

Low-power dividers are optimized to consume minimal energy, making them ideal for battery-powered devices and reducing overall power draw in larger systems.

### **Extended Battery Life:**

In portable electronics like smartphones and wearables, using low-power components extends battery life, improving user experience.

#### Reduced Heat Generation:

Lower power consumption translates to less heat dissipation, which reduces the need for additional cooling solutions and improves the reliability of the device.

### **Enhanced Energy Efficiency:**

By using techniques like clock gating, voltage scaling, and operand gating, low-power dividers ensure only the required energy is used, increasing system efficiency.

### Improved Device Longevity:

Lower operating power reduces wear on circuit components, enhancing the lifespan of the device, especially in applications where high-performance tasks are regularly performed.

# 5 Disadvantages of Low-Power Divider

### Reduced Speed:

Many low-power techniques trade off performance for energy savings, potentially slowing down division operations, which may not be suitable for high-speed applications.

### Increased Design Complexity:

Implementing low-power strategies like clock gating, pipelining, and power gating requires complex design and control logic, which increases design time and cost.

### Lower Accuracy in Approximate Dividers:

Some low-power dividers use approximation to save energy, which may result in reduced accuracy and may not be suitable for applications requiring high precision.

### Potential Area Overhead:

Power-saving techniques can add extra circuitry (e.g., clock gating cells, power-gating transistors), which may increase the overall area of the divider circuit.

### **Higher Initial Cost:**

Low-power design strategies and specialized low-power components can increase manufacturing costs, which may not be justifiable for all applications.

# 6 Applications of Low-Power Divider

### Mobile and Portable Devices:

Essential in smartphones, tablets, and wearable devices where prolonged battery life is crucial.

#### IoT and Sensor Nodes:

Used in IoT devices, where power-saving is a priority due to limited energy resources, such as battery-powered or energy-harvested nodes.

### **Embedded Systems:**

Ideal for embedded systems in consumer electronics, automotive applications, and industrial controls, where efficient energy usage is required.

#### Medical Devices:

Utilized in portable or implanted medical devices (e.g., heart rate monitors, insulin pumps) where low power ensures device longevity and patient safety.

#### Wireless Communication:

Low-power dividers are used in wireless communication systems for DSP tasks (like filtering, modulation, and error correction) to process data with minimal power.

### AI and Machine Learning Edge Devices:

Employed in AI accelerators and machine learning processors at the edge, where power efficiency is crucial for real-time data processing in resource-constrained environments.

### **Energy-Efficient Computing:**

Relevant for ultra-low-power microprocessors and microcontrollers used in applications that prioritize power over performance, like smart home devices.

### Biomedical Wearables and Implants:

Used in devices that need to operate continuously on small batteries, like health monitors and other wearable biomedical sensors.

## 7 Conclusion

A low-power divider is an essential component for energy-efficient designs, particularly in battery-operated and portable systems. Achieving low power requires a combination of architectural, algorithmic, and technology-level techniques, often customized to the specific needs of the application. By carefully balancing these elements, designers can achieve effective power reduction without significantly impacting performance.

# 8 FAQs

### 1. What is a low-power divider?

A low-power divider is a specialized circuit that performs division operations while minimizing power consumption. It's optimized for energy efficiency, which is critical in applications where power availability is limited, such as portable devices, IoT, and embedded systems.

### 2. How does a low-power divider differ from a standard divider?

Low-power dividers use various techniques, such as clock gating, operand gating, voltage scaling, and approximation, to reduce power usage. Standard dividers prioritize speed and accuracy, whereas low-power dividers often sacrifice some speed or precision to save power.

### 3. What are the main techniques used to reduce power in a low-power divider?

Common techniques include:

- Clock Gating: Disabling the clock signal to idle parts of the circui
- Operand Gating: Turning off logic gates when operands remain unchange
- Voltage and Frequency Scaling: Lowering the operating voltage and frequency to reduce powe

- Power Gating: Shutting off power to unused sections to reduce leakage powe
- Approximation: Reducing calculation precision in applications where minor errors are acceptable.

### 4. What are the benefits of using a low-power divider in portable devices?

In portable devices, low-power dividers help extend battery life, reduce heat generation, and enhance user experience by allowing devices to perform efficiently without frequent charging.

### 5. What are the trade-offs when using a low-power divider?

- Speed: Low-power designs can be slower due to techniques like voltage scaling and clock gating.
- Accuracy: Approximate computing methods may lead to lower precision.
- Complexity: Design complexity and area might increase due to additional control logic for low-power features.
- Cost: Low-power components can be more expensive than standard ones.

### 6. How does clock gating help reduce power consumption?

Clock gating reduces power by disabling the clock signal to inactive parts of the circuit, thus preventing unnecessary switching. This minimizes dynamic power consumption as only active parts of the divider receive the clock signal.

### 7. Can low-power dividers be used in high-performance applications?

Low-power dividers are generally not ideal for high-performance applications because they may operate at reduced speed or precision. However, they can be used in applications where power is prioritized over speed, or where slight errors are acceptable.

### 8. What applications benefit the most from low-power dividers?

Applications that prioritize energy efficiency, such as IoT devices, mobile devices, biomedical wearables, and embedded systems, benefit the most. Low-power dividers are also useful in edge devices, where power efficiency is critical.

### 9. Are approximate dividers suitable for all low-power applications?

Approximate dividers are suitable when minor errors are acceptable, such as in multimedia processing, sensor data processing, and some AI tasks. For applications that require high accuracy (e.g., scientific computing), approximate dividers may not be ideal.

### 10. How does power-gating work in low-power dividers?

Power-gating involves using transistors to completely disconnect power from parts of the circuit when they are idle. This reduces static (leakage) power, which is particularly important in low-power designs for energy-efficient systems.

### 11. What division algorithms are commonly used in low-power dividers?

Algorithms like non-restoring division, digit recurrence division (e.g., SRT division), and recursive multiplication-based division are common in low-power dividers. These algorithms are chosen for their ability to balance power, speed, and accuracy.

#### 12. How does operand gating reduce power consumption in a divider?

Operand gating reduces dynamic power by turning off parts of the circuit when operands do not change, avoiding unnecessary calculations and switching. This helps in reducing both dynamic and leakage power in the divider.

### 13. Is there a difference in area between standard and low-power dividers?

Yes, low-power dividers may require additional circuitry for power control features like clock gating, operand gating, and power-gating transistors, which can increase the overall area of the circuit.

### 14. What challenges arise when designing a low-power divider?

Challenges include balancing power, speed, and accuracy, as well as dealing with increased complexity due to low-power techniques. Designers must also consider additional area and cost implications of these power-saving methods.

### 15. How can I implement a low-power divider in my design?

To implement a low-power divider, you can start by selecting an efficient division algorithm, apply techniques like clock gating, operand gating, and voltage scaling, and ensure your design is optimized for the specific application's power requirements. Using low-power design tools and libraries can also help.

Created By Team Alpha