

# **Project 70: Latched Comparator**

## **A Comprehensive Study of Advanced Digital Circuits**

**By: Nikunj Agrawal , Gati Goyal, Abhishek Sharma , Ayush Jain**

**Documentation Specialist: Dhruv Patel & Nandini Maheshwari**

Created By Team Alpha

# Contents

|  |          |
|--|----------|
| <b>1 Introduction</b>  | <b>3</b> |
| <b>2 Background</b>  | <b>3</b> |
| <b>3 Structure and Operation</b>   | <b>3</b> |
| 3.1 Structure . . . . .  | 3        |
| 3.2 Operation . . . . .  | 3        |
| <b>4 Implementation in System Verilog</b>  | <b>4</b> |
| <b>5 Simulation Results</b>  | <b>4</b> |
| <b>6 Test Bench</b>  | <b>4</b> |
| <b>7 Schematic</b>   | <b>6</b> |
| <b>8 Advantages and Disadvantages</b>  | <b>6</b> |
| 8.1 Advantages . . . . .   | 6        |
| 8.2 Disadvantages . . . . .  | 7        |
| <b>9 Synthesis Design</b>  | <b>7</b> |
| <b>10 Conclusion</b>   | <b>7</b> |
| <b>11 Frequently Asked Questions (FAQs)</b>  | <b>7</b> |
| 11.1 1. What is a latched comparator? . . . . .                                      | 7        |
| 11.2 2. How does a latched comparator work? . . . . .                                | 8        |
| 11.3 3. What are the common applications of latched comparators? . . . . .           | 8        |
| 11.4 4. What are the advantages of latched comparators? . . . . .                    | 8        |
| 11.5 5. What are the limitations of latched comparators? . . . . .                   | 8        |
| 11.6 6. How do latched comparators differ from other types of comparators? . . . . . | 8        |

# 1 Introduction

Latched comparators are integral components in analog-to-digital converters (ADCs) and various signal processing applications. Unlike dynamic comparators, which operate in a clocked fashion, latched comparators utilize a feedback mechanism to stabilize their output, ensuring that once a comparison is made, the result is held until the next comparison cycle. This stability makes them particularly useful in applications requiring precise voltage comparisons.

The design of latched comparators combines the principles of dynamic logic with feedback latches, allowing them to achieve high speed while maintaining power efficiency. This document provides a comprehensive overview of latched comparators, detailing their architecture, operation, advantages, and applications.

## 2 Background

Latched comparators function by sampling the input voltages and using feedback to ensure that the output remains stable after the comparison. This design approach allows for greater immunity to noise and reduced susceptibility to voltage fluctuations compared to other comparator types.

The key feature of latched comparators is their ability to hold the output state after the evaluation phase, making them well-suited for high-speed applications where input signals may change rapidly. This document will explore the various components and operation phases of latched comparators in detail.

## 3 Structure and Operation

Latched comparators consist of several key components that enable their fast and efficient operation.

### 3.1 Structure

The structure of a latched comparator typically includes:

- **Input Transistors:** The input signals are fed into differential pairs, typically using NMOS or PMOS transistors.
- **Latch Circuit:** A feedback latch holds the output value, providing stability and preventing output fluctuation after comparison.
- **Control Logic:** This controls the timing of the evaluation and latching phases, ensuring proper operation.
- **Output Stage:** The final output is typically a single-ended signal indicating the result of the comparison.

### 3.2 Operation

The operation of a latched comparator can be broken down into several phases:

1. **Input Sampling:** The input voltages are applied to the differential pairs, and the comparator samples the input signals.
2. **Evaluation Phase:** During this phase, the comparator evaluates which input is greater. The differential inputs are compared, and the output state begins to change based on the input conditions.
3. **Latching Phase:** The output is latched to maintain the result of the comparison. The latch ensures that the output state is stable and remains unchanged until the next evaluation cycle.

4. **Reset Phase:** After the output is stable, the circuit resets to prepare for the next comparison cycle.

The latched nature of the operation allows the comparator to achieve high speeds while providing stability against noise and input fluctuations.

## 4 Implementation in System Verilog

Below is an example of a simple latched comparator implemented in System Verilog:

Listing 1: Latched Comparator

```
1  module LatchedComparator (
2      input logic clk,           // Clock signal
3      input logic rst_n,        // Active-low reset
4      input logic [3:0] a,      // Input A
5      input logic [3:0] b,      // Input B
6      output logic a_gt_b,      // Output: A > B
7      output logic a_eq_b,      // Output: A == B
8      output logic a_lt_b       // Output: A < B
9  );
10     // Intermediate registers for latched outputs
11     logic a_gt_b_latch;
12     logic a_eq_b_latch;
13     logic a_lt_b_latch;
14
15     always_ff @(posedge clk or negedge rst_n) begin
16         if (!rst_n) begin
17             a_gt_b_latch <= 0;
18             a_eq_b_latch <= 0;
19             a_lt_b_latch <= 0;
20         end else begin
21             // Compare and latch results
22             a_gt_b_latch <= (a > b);
23             a_eq_b_latch <= (a == b);
24             a_lt_b_latch <= (a < b);
25         end
26     end
27
28     // Assign latched outputs
29     assign a_gt_b = a_gt_b_latch;
30     assign a_eq_b = a_eq_b_latch;
31     assign a_lt_b = a_lt_b_latch;
32 endmodule
```

## 5 Simulation Results

## 6 Test Bench

The following test bench verifies the functionality of the latched comparator:

Listing 2: Latched Comparator Testbench

```
1  module tb_LatchedComparator;
2      logic clk;
3      logic rst_n;
4      logic [3:0] a;
```

 


Figure 1: Simulation results of Latched Comparator

```

5    logic [3:0] b;
6    logic a_gt_b;
7    logic a_eq_b;
8    logic a_lt_b;
9
10   LatchedComparator uut (
11       .clk(clk),
12       .rst_n(rst_n),
13       .a(a),
14       .b(b),
15       .a_gt_b(a_gt_b),
16       .a_eq_b(a_eq_b),
17       .a_lt_b(a_lt_b)
18   );
19
20   initial begin
21       // Initialize signals
22       clk = 0;
23       rst_n = 0;
24       a = 0;
25       b = 0;
26
27       // Apply reset
28       #5 rst_n = 1;
29
30       // Test Case 1: A = 3, B = 2
31       a = 4'd3; b = 4'd2;
32       #10; // Wait for a clock cycle
33
34       // Check results
35       assert(a_gt_b && !a_eq_b && !a_lt_b) else $fatal("Test Case 1
           Failed");
36
37       // Test Case 2: A = 2, B = 2
38       a = 4'd2; b = 4'd2;
39       #10; // Wait for a clock cycle

```

```

40
41 // Check results
42 assert(!a_gt_b && a_eq_b && !a_lt_b) else $fatal("Test Case 2
    Failed");
43
44 // Test Case 3: A = 1, B = 2
45 a = 4'd1; b = 4'd2;
46 #10; // Wait for a clock cycle
47
48 // Check results
49 assert(!a_gt_b && !a_eq_b && a_lt_b) else $fatal("Test Case 3
    Failed");
50
51 // Finish simulation
52 $finish;
53 end
54
55 // Clock generation
56 always #5 clk = ~clk; // 10 time units period
57 endmodule

```

## 7 Schematic

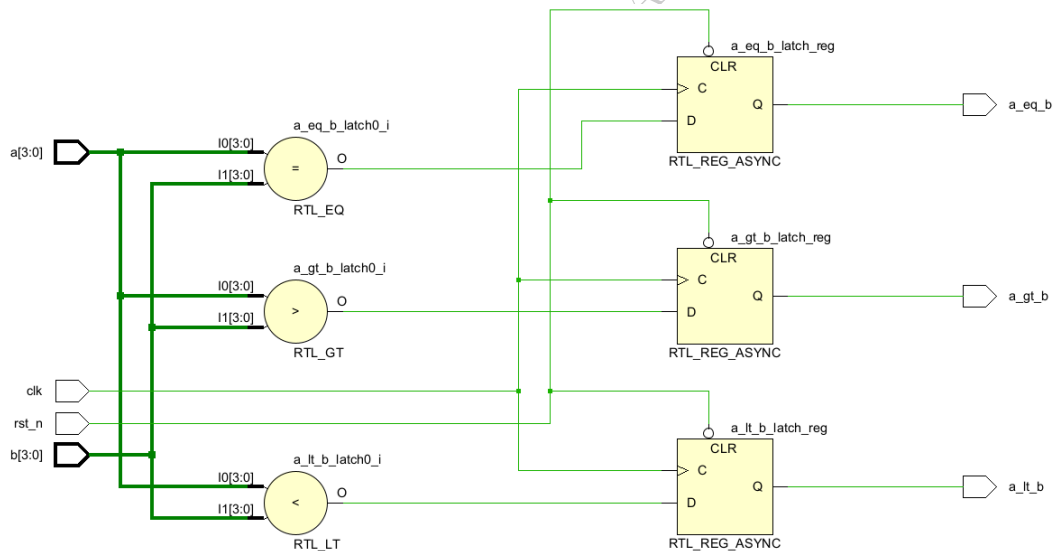


Figure 2: Schematic of Latched Comparator

## 8 Advantages and Disadvantages

Latched comparators offer several advantages and disadvantages that impact their application in electronic systems.

### 8.1 Advantages

- **High Speed:** Latched comparators can achieve rapid response times, making them ideal for high-frequency applications.

- **Noise Immunity:** The feedback mechanism helps stabilize the output against noise, providing reliable comparisons.
- **Stable Output:** Once latched, the output remains stable until the next comparison, reducing uncertainty.

## 8.2 Disadvantages

- **Complexity:** The inclusion of feedback latches can complicate the design and timing analysis.
- **Limited Input Range:** Performance can be affected by the input voltage range, necessitating careful design considerations.
- **Power Consumption:** While generally low, power consumption may increase with more complex feedback mechanisms.

# 9 Synthesis Design

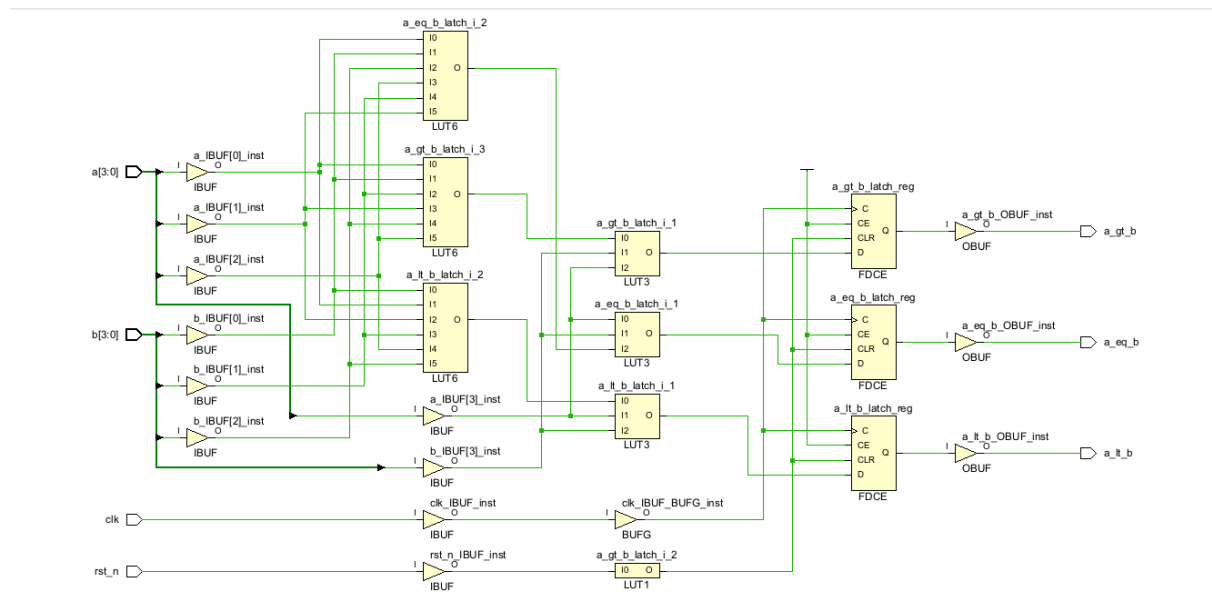


Figure 3: Synthesis of Latched Comparator

## 10 Conclusion

Latched comparators play a crucial role in modern electronic systems, particularly in high-speed and precision applications. Their ability to provide stable and rapid comparisons makes them essential in analog-to-digital conversion and other signal processing tasks.

As technology continues to advance, latched comparators will remain an important area of research and development, driving innovations in speed, accuracy, and reliability. Understanding their design and operational principles is vital for engineers working in electronics and signal processing.

## 11 Frequently Asked Questions (FAQs)

### 11.1 1. What is a latched comparator?

A latched comparator is a circuit that compares two input voltages and holds the output stable until the next comparison, providing high speed and noise immunity.

## **11.2 2. How does a latched comparator work?**

Latched comparators use a feedback mechanism to stabilize their output after the comparison phase, ensuring that the output remains unchanged until the next evaluation.

## **11.3 3. What are the common applications of latched comparators?**

Common applications include:

- Analog-to-Digital Converters (ADCs)
- Signal Processing Circuits
- High-Speed Data Acquisition Systems

## **11.4 4. What are the advantages of latched comparators?**

Advantages include high speed, noise immunity, and stable output.

## **11.5 5. What are the limitations of latched comparators?**

Limitations may include design complexity, a limited input range, and potentially higher power consumption in complex designs.

## **11.6 6. How do latched comparators differ from other types of comparators?**

Latched comparators hold their output state after comparison, whereas other types, like dynamic comparators, may not provide the same level of stability.

Created by Team Alpha