

Project 91:Mealy Machine for Bit Parity Checker

A Comprehensive Study of Advanced Digital Circuits

By: Abhishek Sharma , Ayush Jain , Gati Goyal, Nikunj Agrawal

Documentation Specialist: Dhruv Patel & Nandini Maheshwari

Created By Team Alpha

Contents

1 Project Overview	3
2 Mealy Machine for Bit Parity Checker	3
2.1 Key Components of Mealy Machine for Bit Parity Checker	3
2.2 Working of Mealy Machine for Bit Parity Checker	4
2.3 RTL Code	5
2.4 Testbench	6
3 Results	7
3.1 Simulation	7
3.2 Schematic	7
3.3 Synthesis Design	8
4 Advantages of Mealy Machine for Bit Parity Checker	8
5 Disadvantages of Mealy Machine for Bit Parity Checker	8
6 Applications of Mealy Machine for Bit Parity Checker	9
7 Conclusion	9
8 FAQs	10

Created By Team Alpha

1 Project Overview

The Mealy Machine for Bit Parity Checker checks the parity of a bit stream, generating an output based on whether the count of 1s is even or odd. It has two states: S0 (Even Parity) and S1 (Odd Parity), with transitions based on input bits (0 or 1). The output, unlike in a Moore machine, depends on both the current state and input bit, providing an immediate response. Implemented using Verilog/VHDL, the design includes a state diagram, state table, and testbench. This project has applications in error detection, communication systems, and embedded systems.

2 Mealy Machine for Bit Parity Checker

2.1 Key Components of Mealy Machine for Bit Parity Checker

A Mealy Machine is a finite-state machine where the outputs depend on both the current state and the input. In the case of a Bit Parity Checker, the machine monitors a serial bit stream and generates a parity bit based on whether the total number of 1s encountered in the stream is even or odd. Below are the key components involved in the design of a Mealy machine for bit parity checking.

States

- **S0 (Even Parity State):** This state indicates that the cumulative number of 1s encountered so far is even.
- **S1 (Odd Parity State):** This state indicates that the cumulative number of 1s encountered so far is odd.
- These two states are sufficient to track whether the parity is even or odd. The state transitions are controlled by the incoming bits, which cause the machine to either stay in the current state or transition to the other state.

Inputs

- The machine accepts a serial bit stream as input, which consists of binary digits (0s and 1s).
- The input at each clock cycle will trigger the state transition logic.

Outputs

- The output, which is the parity bit, is determined by both the current state and the input bit, which is a defining feature of the Mealy machine.
- If the machine is in S0, the output will be 0 (indicating even parity).
- If the machine is in S1, the output will be 1 (indicating odd parity).
- This immediate output generation based on both the state and input distinguishes the Mealy machine from the Moore machine, where outputs are solely based on the state.

State Transition Logic

- The state transitions are governed by the following logic:
 - **From S0:**
 1. Input = 0 \rightarrow Stay in S0 (parity remains even).
 2. Input = 1 \rightarrow Transition to S1 (parity becomes odd).
 - **From S1:**
 1. Input = 0 \rightarrow Stay in S1 (parity remains odd).
 2. Input = 1 \rightarrow Transition to S0 (parity becomes even).

- The state transitions depend on both the current state and the incoming input bit, ensuring the output is generated immediately based on these two factors.

Clock and Control Signals

- The machine operates synchronously, with transitions occurring on each clock cycle. The clock signal triggers the state transitions and ensures that the output is updated correctly with every input bit.

Flip-Flops for State Storage

- Flip-flops (usually D-type flip-flops) are used to store the current state of the machine. The flip-flops hold the state until the next clock cycle, and their outputs feed into the transition logic to determine the next state.

Combinational Logic for Transitions and Outputs

- Combinational logic calculates the next state and the output based on the current state and input. The next state is derived from the current state and input, and the output is determined based on the current state and input bit, according to the transition logic table.

2.2 Working of Mealy Machine for Bit Parity Checker

The Mealy Machine for a Bit Parity Checker operates by monitoring a stream of input bits and determining whether the number of 1s in the stream is even or odd. The machine uses two states: S0 (Even Parity) and S1 (Odd Parity). It transitions between these states based on the input bits, updating the parity each time a new bit is processed. The key feature of a Mealy machine is that the output is determined by both the current state and the input bit, providing a responsive output immediately after each input is received.

The state transitions work as follows: when in S0 (Even Parity), if the input bit is 0, the machine remains in S0 (parity remains even). If the input bit is 1, it transitions to S1 (Odd Parity). Conversely, in S1 (Odd Parity), a 0 keeps the machine in S1, while a 1 will transition it back to S0. The output at each state is determined by both the state and the input: S0 produces an output of 0 (even parity), and S1 produces an output of 1 (odd parity).

This design allows for continuous tracking of the bit stream, updating the parity bit with each new input. For example, given an input stream like 101010, the machine alternates between the states, outputting 1 1 0 0 1 1, reflecting the changing parity after each bit. The Mealy machine's ability to immediately generate output based on both the current state and input makes it an efficient and responsive solution for error detection in communication systems.

2.3 RTL Code

Listing 1: Mealy Machine for Bit Parity Checker

```
1
2 module mealy_bit_parity_checker (
3     input logic clk, reset,
4     input logic bit_in,          // Serial input bit stream
5     output logic parity_bit      // Output: 1 for even parity, 0
6     otherwise
7 );
8
9 // Define states
10 typedef enum logic {EVEN, ODD} state_t;
11 state_t current_state, next_state;
12
13 // State transition logic
14 always_ff @(posedge clk or posedge reset) begin
15     if (reset)
16         current_state <= EVEN; // Start with even parity
17     else
18         current_state <= next_state;
19 end
20
21 // Next state and output logic (Mealy output depends on state and
22 // input)
23 always_comb begin
24     next_state = current_state;
25     case (current_state)
26         EVEN: begin
27             next_state = (bit_in) ? ODD : EVEN; // Flip to ODD on
28             bit_in = 1
29             parity_bit = 1;                      // Output 1 for
30             even parity
31         end
32         ODD: begin
33             next_state = (bit_in) ? EVEN : ODD; // Flip to EVEN on
34             bit_in = 1
35             parity_bit = 0;                      // Output 0 for odd
36             parity
37         end
38     endcase
39 end
40 endmodule
```

2.4 Testbench

Listing 2: Mealy Machine for Bit Parity Checker

```
1
2 module tb_mealy_bit_parity_checker();
3     logic clk, reset;
4     logic bit_in;
5     logic parity_bit;
6
7     mealy_bit_parity_checker uut (
8         .clk(clk),
9         .reset(reset),
10        .bit_in(bit_in),
11        .parity_bit(parity_bit)
12    );
13
14    // Clock generation
15    initial begin
16        clk = 0;
17        forever #5 clk = ~clk; // 10ns clock period
18    end
19
20    // Test scenario
21    initial begin
22        reset = 1; bit_in = 0; // Start with reset asserted
23        #10 reset = 0;        // Deassert reset
24
25        // Apply serial input bits
26        #10 bit_in = 1; // Transition to ODD
27        #10 bit_in = 0; // Stay in ODD
28        #10 bit_in = 1; // Transition to EVEN
29        #10 bit_in = 1; // Transition to ODD
30        #10 bit_in = 0; // Stay in ODD
31        #10 bit_in = 1; // Transition to EVEN
32
33        #50 $stop; // Stop simulation
34    end
35
36    // Monitor outputs
37    initial begin
38        $monitor("Time: %0t | Bit In: %b | Parity Bit: %b | Current
39                State: %s",
40                $time, bit_in, parity_bit, uut.current_state.name());
41    end
42 endmodule
```

3 Results

3.1 Simulation

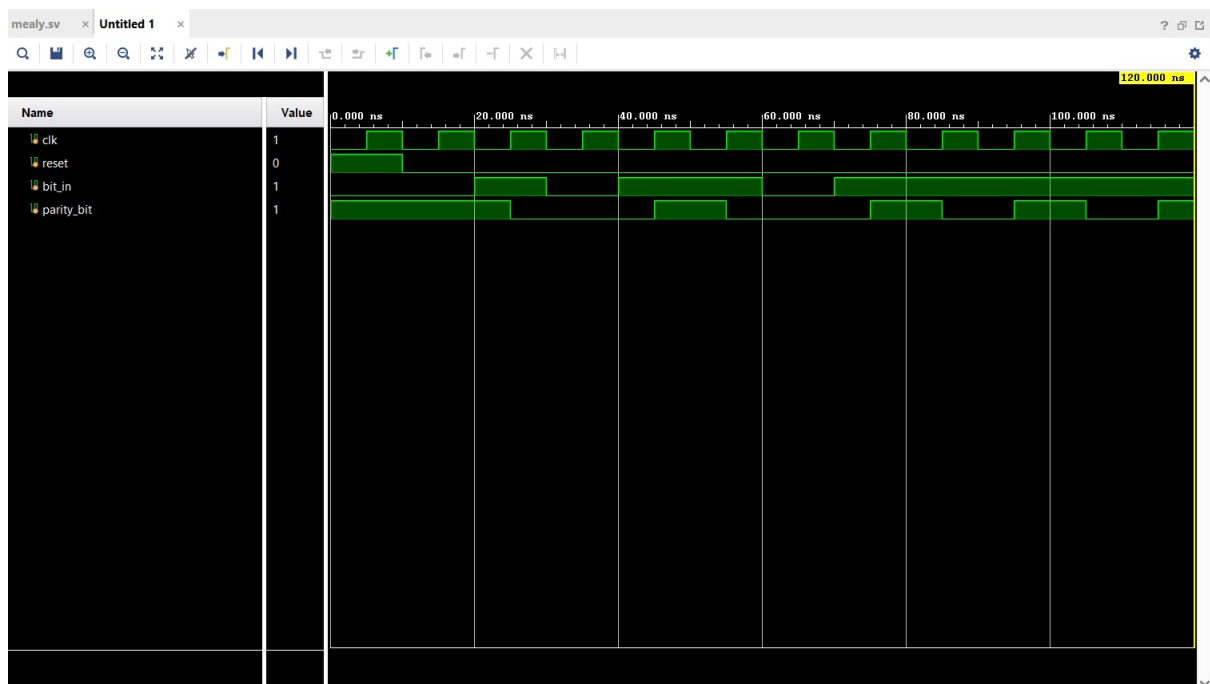


Figure 1: Simulation of Mealy Machine for Bit Parity Checker

3.2 Schematic

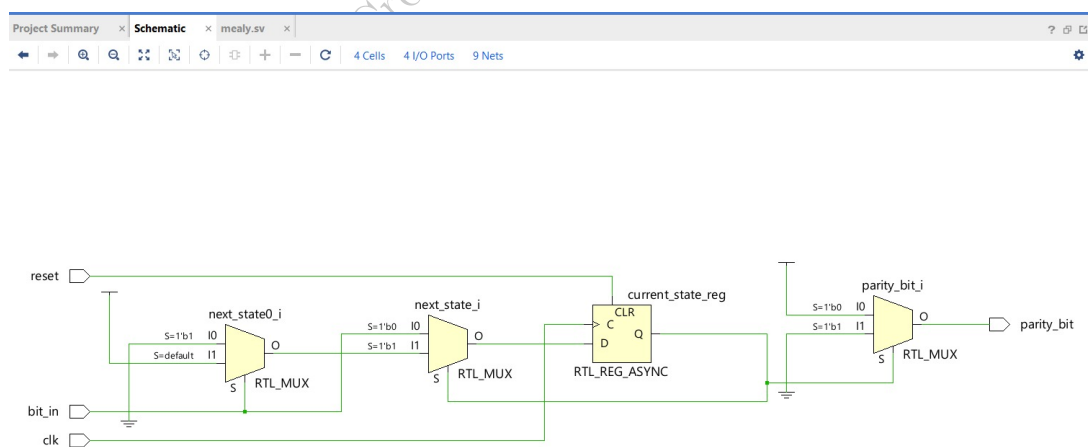


Figure 2: Schematic of Mealy Machine for Bit Parity Checker

3.3 Synthesis Design

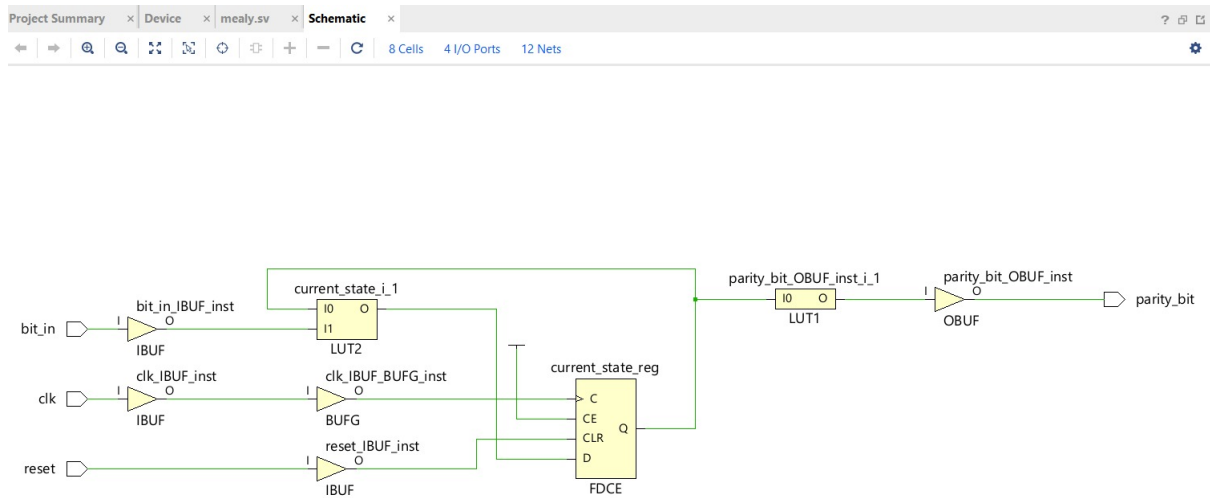


Figure 3: Synthesis Design of Mealy Machine for Bit Parity Checker

4 Advantages of Mealy Machine for Bit Parity Checker

- **Immediate Output:** The output is generated immediately based on both the current state and input, providing real-time feedback.
- **Efficiency:** Requires fewer states and transitions compared to other models like Moore machines, making it more efficient.
- **Responsive:** The design reacts quickly to input changes, ensuring fast parity checking.
- **Simple Design:** The state transition logic is straightforward, making it easy to implement in hardware using tools like Verilog or VHDL.
- **Compact Hardware:** Less complex than alternative designs, requiring fewer resources in hardware implementations, such as FPGAs.

5 Disadvantages of Mealy Machine for Bit Parity Checker

- **Complexity in Output Timing:** Since output depends on both the state and input, it can lead to timing issues or glitches in asynchronous designs.
- **Less Predictable Output:** The output changes immediately with each input, which may be less intuitive than the state-based output of a Moore machine.
- **Harder to Debug:** The combined dependence on state and input for outputs can make debugging more challenging, especially in large systems.
- **Potential for Noise Sensitivity:** Immediate output changes may cause the system to be more susceptible to noise or glitches in input signals.

6 Applications of Mealy Machine for Bit Parity Checker

Error Detection in Communication Systems:

- Used in data transmission protocols (e.g., UART, Ethernet) to detect transmission errors by generating parity bits to ensure data integrity.

Memory Systems:

- Helps in memory modules (e.g., DRAM) to detect and correct errors in data stored or retrieved, ensuring reliable operations.

Digital Circuit Design:

- Used in circuits where real-time parity checking is required, such as in communication interfaces and data bus systems.

Embedded Systems:

- Applied in resource-constrained embedded systems for lightweight error checking, ensuring reliable communication with minimal overhead.

Computer Architecture:

- Utilized in CPU design to detect errors in data paths, ensuring safe data transfers and processing.

Cryptography and Security Systems:

- Parity checkers can be used in secure data exchanges to verify the correctness of transmitted information and prevent data tampering.

7 Conclusion

The Mealy machine for bit parity checking efficiently generates a parity bit based on the input stream and its current state. Each bit causes an immediate transition and output, providing real-time parity checking. The output depends on both the current state and the input bit, making the system highly responsive. This mechanism is particularly useful for real-time error detection in communication systems.

8 FAQs

What is a Mealy machine?

- A Mealy machine is a type of finite-state machine where the output depends on both the current state and the input, unlike a Moore machine, where the output depends only on the current state.

What does a bit parity checker do?

- A bit parity checker determines if the number of 1s in a binary stream is even or odd. It generates a parity bit that reflects this count, which helps in error detection.

How does the Mealy machine work for bit parity checking?

- The Mealy machine keeps track of the parity (even or odd) of the input stream using two states: S0 for even parity and S1 for odd parity. The output is determined by both the current state and the incoming bit.

What are the advantages of a Mealy machine for this task?

- It offers immediate output, is efficient in design, and provides real-time response to input changes, making it suitable for real-time error detection in systems like communication protocols.

What are the disadvantages of using a Mealy machine for bit parity checking?

- The immediate output can lead to timing issues, making the system potentially more susceptible to glitches. It may also be harder to debug and less predictable than Moore machines.

Where is the Mealy machine for bit parity checker applied?

- It is widely used in communication systems, memory systems, digital circuit design, embedded systems, computer architecture, and cryptography to ensure data integrity and error detection.

What tools are used to implement the Mealy machine?

- The Mealy machine can be implemented using hardware description languages like Verilog or VHDL, and tools like ModelSim or Xilinx Vivado for simulation and synthesis.

How does the output of a Mealy machine differ from that of a Moore machine?

- In a Mealy machine, the output is generated immediately based on both the current state and input, while in a Moore machine, the output depends solely on the state.