

# **Project 36 : Fixed Multiplier**

## **A Comprehensive Study of Advanced Digital Circuits**

**By: Abhishek Sharma , Ayush Jain , Gati Goyal, Nikunj Agrawal**

**Documentation Specialist: Dhruv Patel & Nandini Maheshwari**

Created By Team Alpha

# Contents

<b>1 Project Overview</b>	<b>3</b>
<b>2 Fixed Multiplier</b>	<b>3</b>
2.1 Description . . . . .	3
2.2 Components of a Fixed Multiplier: . . . . .	3
<b>3 How it works ?</b>	<b>3</b>
<b>4 Implementation</b>	<b>4</b>
4.1 RTL Code . . . . .	4
4.2 Testbench . . . . .	4
<b>5 Results</b>	<b>5</b>
5.1 Simulation . . . . .	5
5.2 Schematic . . . . .	5
5.3 Synthesis Design . . . . .	6
<b>6 Comparison with Other Multiplier:</b>	<b>6</b>
<b>7 Advantages, Disadvantages and Applications</b>	<b>7</b>
7.1 Advantages of the Fixed Multiplier: . . . . .	7
7.2 Disadvantages of the Fixed Multiplier: . . . . .	7
7.3 Applications of the Fixed Multiplier: . . . . .	7
<b>8 FAQs</b>	<b>8</b>

Created By Team Alpha

# 1 Project Overview

A fixed multiplier refers to a circuit or component that multiplies an input signal by a constant value. This concept is applied in various areas like frequency multipliers, which generate an output signal with a frequency that is an integer multiple of the input, or in amplifiers, where the input signal's amplitude is multiplied by a fixed gain. Fixed multipliers are also used in digital signal processing to scale digital values. Voltage multipliers, like the Cockcroft-Walton multiplier, increase AC voltage to higher DC levels using capacitors and diodes to achieve a fixed voltage multiplication.

## 2 Fixed Multiplier

### 2.1 Description

A fixed multiplier in electronics is a circuit or device that scales an input signal, such as voltage, current, or frequency, by a constant, predetermined factor. It is used in various applications, including frequency multipliers, which generate higher frequencies by multiplying the input signal's frequency by a fixed integer value. This is common in RF and communication systems to achieve high-frequency signals. In amplifiers, the fixed multiplier refers to the gain, where the input signal is amplified by a specific amount. Voltage multipliers, like the Cockcroft-Walton circuit, convert low AC voltage into higher DC voltage by using capacitors and diodes. Similarly, in digital signal processing, fixed multipliers scale digital values by a constant factor to modify signal characteristics. These systems are designed to consistently produce predictable and stable output based on a fixed input-to-output ratio.

### 2.2 Components of a Fixed Multiplier:

#### Frequency Multipliers:

- Non-linear Devices: Diodes, transistors.
- Bandpass Filters: Select desired harmonics.
- Amplifiers: Boost the multiplied signal.

#### Amplifiers (Fixed Gain):

- Transistors (BJT, FET): For amplification.
- Resistors: Set gain.
- Capacitors: For signal stabilization.

#### Voltage Multipliers:

- Diodes: Direct charge flow.
- Capacitors: Store and increase voltage.

#### Digital Multipliers (DSP):

- Logic Gates: Perform digital multiplication.
- Registers: Store intermediate values.

## 3 How it works ?

A fixed multiplier works by consistently scaling an input signal by a predetermined constant factor, utilizing different mechanisms based on its type:

- **Frequency Multipliers:** Non-linear devices (diodes/transistors) generate harmonics of the input frequency, and bandpass filters select the desired harmonic while amplifiers boost the output.

- **Amplifiers:** Transistors amplify the input signal by a fixed gain determined by resistor ratios in the circuit, resulting in an output that is a constant multiple of the input.
- **Voltage Multipliers:** Circuits use capacitors and diodes to charge and accumulate voltage, effectively increasing the output voltage based on the number of stages.
- **Digital Multipliers:** Logic gates perform bit-wise operations on binary numbers, multiplying the input by a fixed constant and storing intermediate results in registers.

In all cases, the output signal is a reliable multiple of the input based on the design of the multiplier.

## 4 Implementation

### 4.1 RTL Code

Listing 1: Fixed Multiplier

```

1
2
3 module fixed_multiplier #(parameter WIDTH = 8, MULTIPLICAND = 8'd10) (
4     input  logic [WIDTH-1:0] A, // 8-bit input A
5     output logic [15:0] product // 16-bit product
6 );
7     always_comb begin
8         product = A * MULTIPLICAND; // Fixed multiplicand
9     end
10 endmodule

```

### 4.2 Testbench

Listing 2: Fixed Multiplier

```

1
2 module tb_fixed_multiplier;
3     logic [7:0] A;
4     logic [15:0] product;
5
6     fixed_multiplier #(8, 8'd10) uut (.A(A), .product(product)); //
7     Fixed multiplicand of 10
8
9     initial begin
10        // Test case 1
11        A = 8'd25;
12        #10;
13        $display("A = %d, Product = %d", A, product);
14
15        // Test case 2
16        A = 8'd100;
17        #10;
18        $display("A = %d, Product = %d", A, product);
19
20        $finish;
21    end
22 endmodule

```

## 5 Results

### 5.1 Simulation

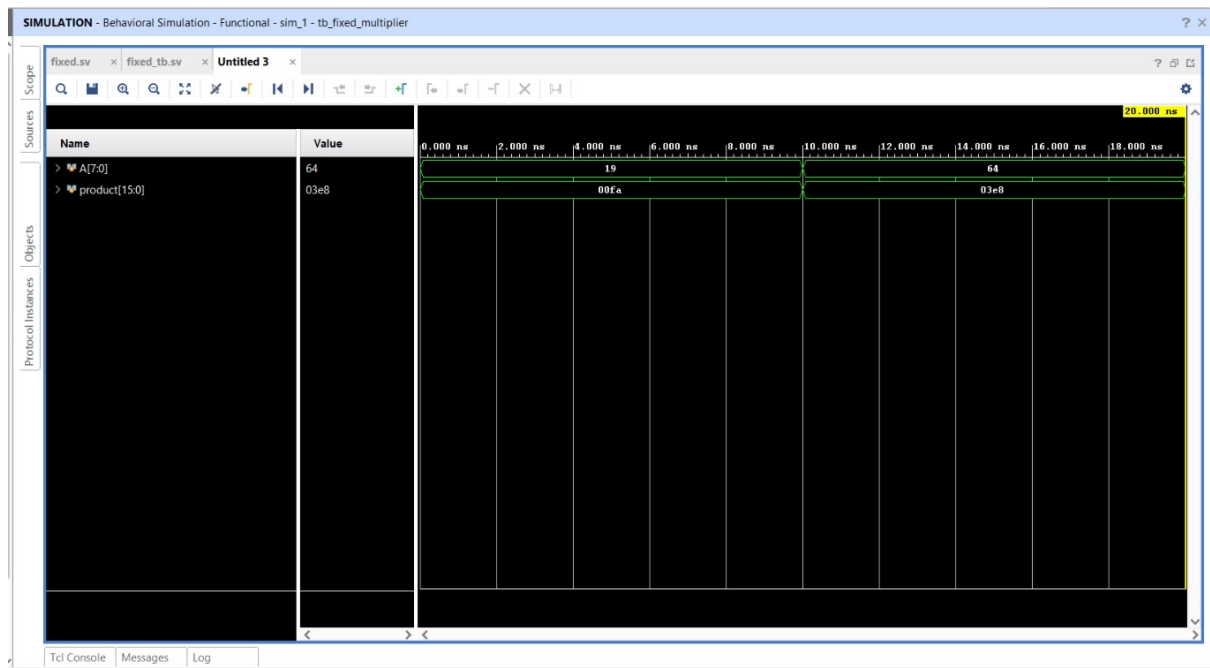


Figure 1: Simulation of Fixed Multiplier

### 5.2 Schematic

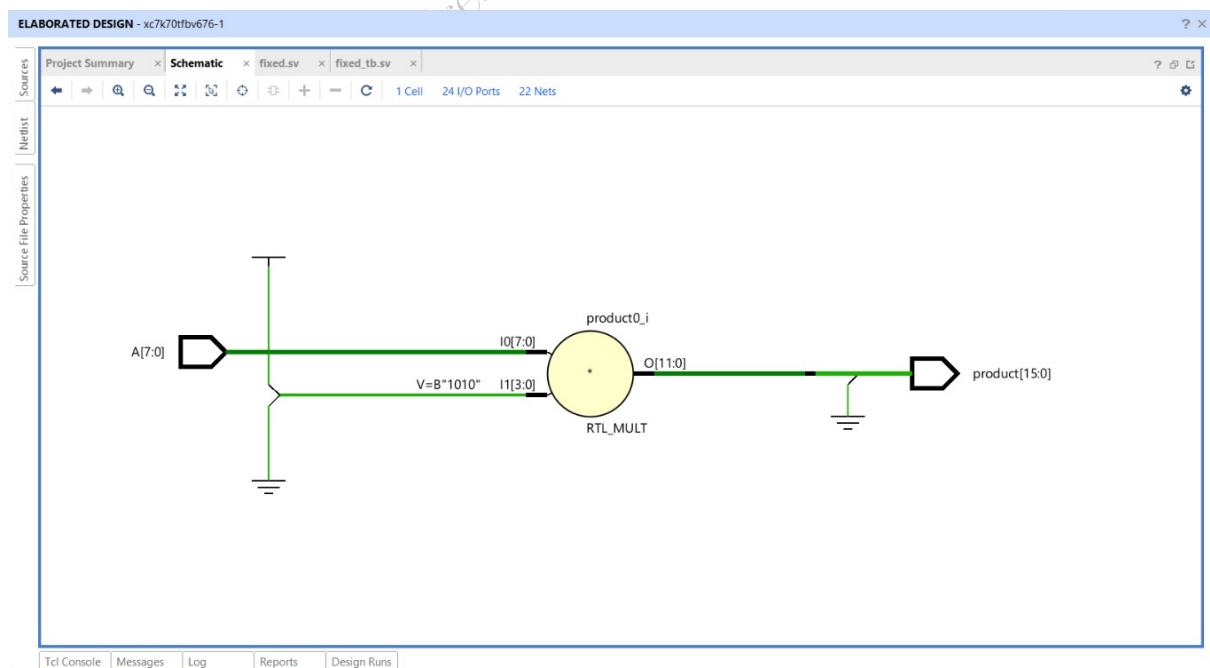


Figure 2: Schematic of Fixed Multiplier

## 5.3 Synthesis Design

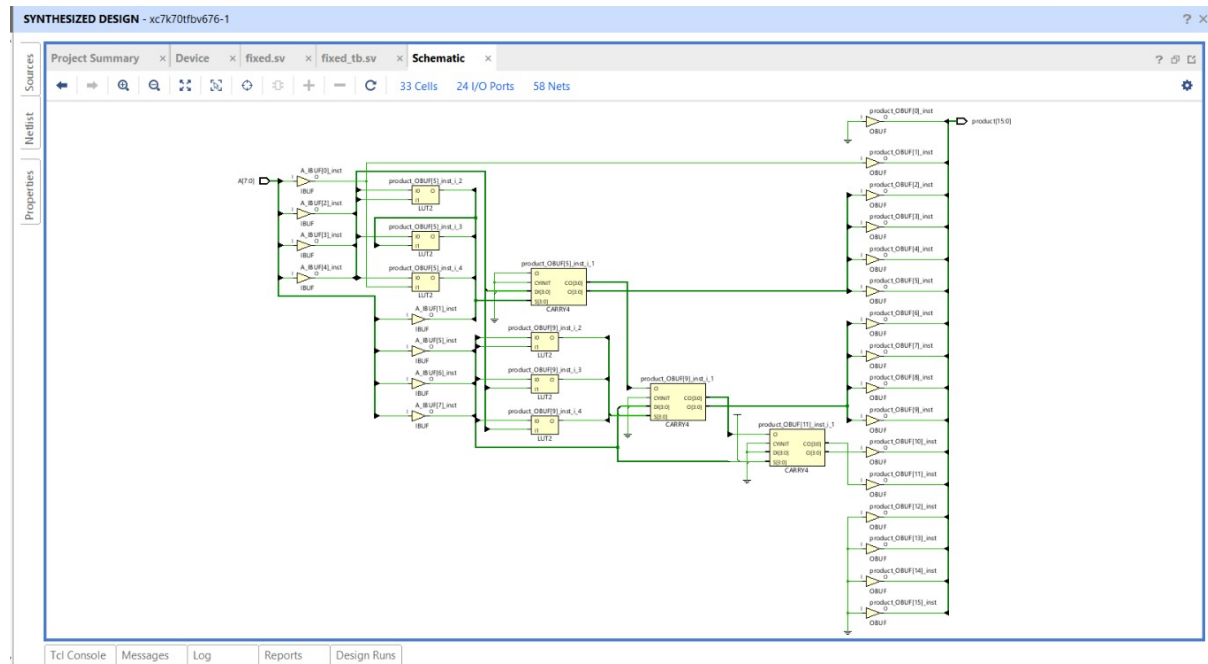


Figure 3: Synthesis Design of Fixed Multiplier

## Explanation

A fixed multiplier in electronics is a circuit or device designed to scale an input signal—such as voltage, current, or frequency—by a constant, predetermined factor. Various types of fixed multipliers serve different functions. Frequency multipliers generate an output frequency that is a fixed multiple of the input frequency using non-linear devices, like diodes, along with filters to select the desired harmonics. Amplifiers with fixed gain amplify input signals by a consistent gain determined by resistor ratios, resulting in predictable output amplitudes. Voltage multipliers convert low AC voltages into higher DC voltages using capacitors and diodes to progressively accumulate voltage. Finally, digital multipliers perform multiplication of binary numbers in digital signal processing using logic gates, producing outputs that are fixed multiples of the inputs. Overall, fixed multipliers play a crucial role in providing reliable signal scaling across various electronic applications.

## 6 Comparison with Other Multiplier:

- **Variable Multiplier:** A fixed multiplier multiplies an input signal by a constant factor, ensuring reliable and consistent output for applications like frequency multiplication and fixed-gain amplifiers. It features a simple design using fewer components. In contrast, a variable multiplier allows the multiplication factor to be dynamically adjusted, making it ideal for flexible applications like audio processing. However, it is more complex to implement and can lead to less predictable output due to its adjustable nature.
- **Digital Multiplier:** A fixed multiplier operates in analog domains, multiplying signals by a constant factor and is commonly used in amplifiers and voltage converters. It involves passive components and is straightforward to implement. Conversely, a digital multiplier performs multiplication on binary numbers using logic circuits, essential for digital signal processing and computing. While fixed multipliers are generally faster, digital multipliers enable complex calculations and precise control.

## 7 Advantages, Disadvantages and Applications

### 7.1 Advantages of the Fixed Multiplier:

- **Simplicity:** Fixed multipliers have straightforward designs, often using fewer components, which makes them easier to implement and troubleshoot.
- **Predictability:** They provide consistent and reliable outputs since the multiplication factor is constant, ensuring predictable performance across various applications.
- **Speed:** Fixed multipliers typically operate faster than their variable counterparts because they do not require adjustments or additional processing to change the multiplication factor.
- **Stability:** The fixed gain or multiplication factor results in stable performance over time, minimizing the effects of drift or variation in components.
- **Cost-Effectiveness:** Due to their simpler design and fewer components, fixed multipliers can be more cost-effective in manufacturing and deployment compared to more complex variable multipliers.
- **Lower Power Consumption:** Fixed multipliers generally consume less power than variable systems, especially in applications where minimal energy use is essential.
- **Ease of Calibration:** Calibration is simpler since the multiplication factor does not change, making maintenance and adjustments straightforward.
- **High Linearity:** Fixed multipliers often exhibit better linearity in signal processing, making them ideal for applications requiring high fidelity in the output signal.

### 7.2 Disadvantages of the Fixed Multiplier:

- **Lack of Flexibility:** Fixed multipliers operate with a constant multiplication factor, making them unsuitable for applications that require dynamic adjustments or variable scaling of the input signal.
- **Limited Application Range:** Their fixed nature may limit their use in scenarios where a range of multiplication factors is needed, such as in certain audio processing or signal modulation applications.
- **Overhead in Design:** In some cases, achieving a specific fixed multiplication factor may require additional components or complexity, particularly in high-frequency or high-precision applications.
- **Performance Variability:** While they are generally stable, fixed multipliers can be affected by temperature variations, aging components, and other environmental factors, which may impact performance over time.
- **Signal Distortion:** Depending on the design, fixed multipliers may introduce signal distortion, especially when handling signals with large dynamic ranges or nonlinear characteristics.

### 7.3 Applications of the Fixed Multiplier:

- **RF and Microwave Communication:** Frequency multipliers are used to generate higher frequencies from a lower input frequency, making them critical in radio frequency (RF) and microwave communication systems.
- **Amplifiers:** Fixed-gain amplifiers use fixed multipliers to amplify signals by a constant factor, ensuring stable amplification in audio equipment, communication systems, and sensor circuits.
- **Voltage Doublers and Multipliers:** Used in power supplies and high-voltage circuits, voltage multipliers (such as voltage doublers or triplers) convert a low AC input into higher DC output, often in devices like CRTs or medical equipment.

- **Signal Processing:**In analog signal processing, fixed multipliers are employed to scale signals in systems requiring predictable signal enhancement, like in control systems or instrumentation.
- **Oscillators and Signal Generators:**Fixed multipliers are used in oscillators and signal generators to produce harmonic frequencies, which are vital in test equipment and frequency synthesis.
- **Digital Systems:**In digital-to-analog converters (DACs), fixed multipliers ensure consistent signal scaling, providing accurate output levels for digital data.
- **Measurement and Instrumentation:**Fixed multipliers are integral in precision measurement systems, where consistent signal multiplication is necessary for accurate readings, such as in oscilloscopes or signal analyzers.
- **Control Systems:**In feedback control systems, fixed multipliers are used to consistently scale feedback signals, helping to maintain system stability.
- **Telecommunication:**Fixed multipliers are applied in modulators for stable signal transmission in telecommunication systems, ensuring reliable signal strength and frequency.
- **Power Electronics:**Used in AC-DC converters and rectifiers, fixed multipliers assist in converting and managing power efficiently in industrial electronics and consumer appliances.

## 8 FAQs

### • Q1. What is a Fixed Multiplier?

**Answer:** A fixed multiplier in electronics is a circuit or device designed to multiply an input signal—such as voltage, current, or frequency—by a constant, predetermined factor. This means that regardless of variations in the input signal, the output will consistently be a specific multiple of that input.

### • Q2.How does a fixed multiplier work?

**Answer:** It uses components like resistors, capacitors, and diodes to scale the input signal consistently.

### • Q3.What are the types of fixed multipliers?

**Answer:** Common types include frequency multipliers, voltage multipliers, and fixed-gain amplifiers.

### • Q4.What are the applications of fixed multipliers?

**Answer:** Applications include communication systems, power supplies, audio processing, and signal conditioning.

### • Q5.What are the advantages of fixed multipliers?

**Answer:** They offer simplicity, predictability, speed, stability, and cost-effectiveness.

### • Q6. What are the disadvantages of fixed multipliers?

**Answer:** Limitations include lack of flexibility, performance variability, and potential signal distortion.

### • Q7. How do fixed multipliers differ from variable multipliers?

**Answer:** Fixed multipliers have a constant factor, while variable multipliers allow dynamic adjustment of the multiplication factor.

### • Q8. Can fixed multipliers be used in digital circuits?

**Answer:** Yes, fixed multipliers can be utilized in digital systems for tasks requiring constant scaling.

### • Q9. What components are commonly used in fixed multipliers?

**Answer:** Typical components include operational amplifiers, resistors, capacitors, and diodes.

### • Q10. Are fixed multipliers efficient in terms of power consumption?

**Answer:** Generally, fixed multipliers consume less power than variable systems, making them efficient for many applications.